



IES/GATE

←————→
Electrical Engineering

Volume - 6

Analog Electronics



INDEX

S No.	Chapter Title	Page No.
1	Diodes Circuits	1
2	Bipolar Junction Transistor	64
3	Field Effect Transistor	148
4	Operational Amplifier and Application	171
5	Power Amplifier	269
6	Feedback Amplifier	288
7	Timer, Regulators & Filters	317
8	Sinusoidal Oscillators	346

1 CHAPTER


Diodes Circuits

THEORY

1.1 BIASING


A diode can be biased in 2 ways, i.e., forward bias and reverse bias.

Forward Bias :

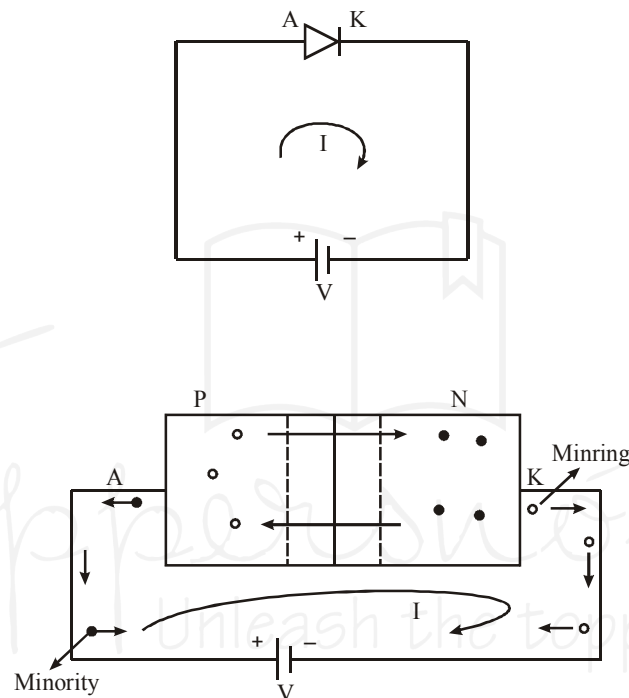

- The anode is connected to the positive terminal and cathode is connected to the negative terminal of the supply.
- The free carriers can cross over to the other side of the depletion layer when the applied forward bias voltage is just above the knee voltage.
- In this the free carrier are diffused across the junction and minority carriers are moving towards the battery.
- The depletion layer width, can become minimum.
- For a small change in the forward bias volume, there is a larger recombination of free carriers and there by the current is increasing exponentially.
- The forward bias voltage not only increase the energy of the free carriers, but also make the covalent bonds to break on both sides of the junction.

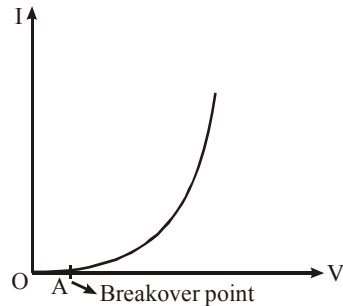- With the applied forward bias, the number of free carriers less due to recombination can be generated due to breakage of covalent bonds.
- The diode can act like a closed switch.
- The V-I characteristics of the diode is a exponential growth and it can out like a non-linear device.



Forward current


$$I_f = I_0 (e^{V_d/\eta V_T} - 1)$$

$$V_T = \frac{kT}{q} = \frac{T}{11600}$$

$$I_f \approx I_0 e^{V_d/\eta V_T}$$

where v_d = voltage across diode
 $\eta = 1$ for Ge, 2 for Si

Reverse Bias :

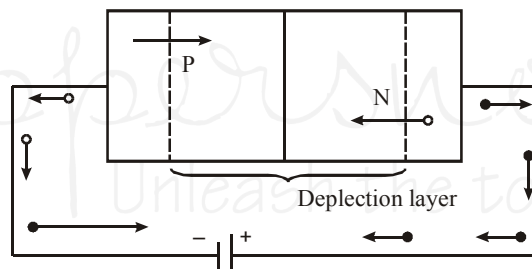

- The anode is converted to the negative terminal and the cathode connected to the positive terminal of the supply.
- The free carriers, i.e., e^- s on n-side and holes on p-side are depleted (moving away) from the junction and move towards battery.
- The width of the depletion layer is increasing as increase in the reverse bias voltage.
- The minority carriers, i.e., holes on n-side and electrons on p-side can diffuse towards the junction.
- The current due to the free carriers is zero.
- The current is flowing due to the recombination of minority carriers and is of the order of ' μA ' for Si.
- This minority current is also called reverse saturation current ' I_0 ' (or) ' I_s '.
- The reverse current is independent of reverse bias volume and depend on temperature strongly.
- The reverse current doubles for every $10^\circ C$ increase in temperature in Ge, where as in Si, it almost doubles for every $6^\circ C$ increase in temperature
- In a R.B. the diode can out like a open switch.

- Equation of current in reverse bias

$$\therefore I_f = I_0 [e^{V_d/\eta V_T} - 1]$$

where V_d = Voltage across diode

= positive for forward bias

= negative for reverse bias


$$I_r = I_0 (e^{-V/\eta V_T} - 1)$$

$$\therefore e^{-V/\eta V_T} \ll 1$$

$$I_r \approx -I_0$$

(-) sign indicates that it is reverse bias and the current in reverse bias is independent of reverse bias voltage and depending strongly on temperature.

V-I characteristics :

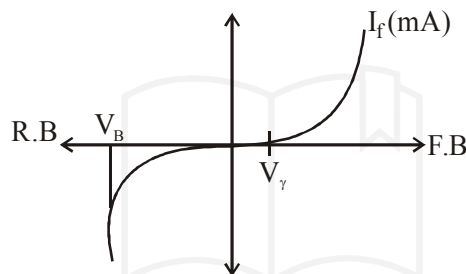

Temperature Dependence of V-I characteristics : Reverse saturation current approximately doubles for every 10° rise in temperature if $I_0 = I_{01}$ at $T = T_1$, then at temperature T , I_0 is

$$I_0(T) = I_{01} \times 2^{(T-T_1/10)}$$


1.2 DIODE RESISTANCE

A resistance of a diode can be expressed in terms of static and dynamic.

Static (or) DC Resistance : It is expressed as the ratio of the voltage to the corresponding current at a given point of characteristic.


$$R_{DC} = \frac{V}{I} (\Omega)$$

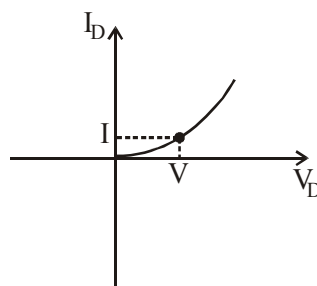The static resistance is valid only for linear devices, but diode is a non linear device.



Dynamic (or) AC Resistance : The dynamic resistance is not constant and mainly depending on the operating voltage region.

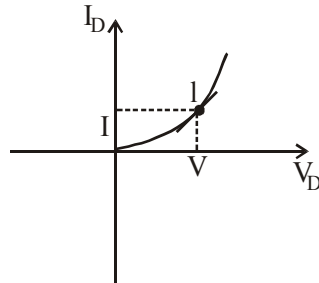The dynamic resistance is expressed as the reciprocal of the slope of the characteristic.



$$r_c = \frac{1}{\text{slope}} = \frac{1}{dI/dV} = \frac{dV}{dI} \Omega$$

$$r_{AC} = \frac{dV}{dI} = \frac{\eta K T}{qI} = \frac{\eta r_T}{I} \Omega$$

$$\therefore r_{AC} \propto \frac{1}{I}$$



For Ge at $T = 300 \text{ k}$ (room temperature)

$$r_{AC} = \frac{26}{I} \Omega \quad [\because \eta = 1, T = 300\text{k}, V_T = 26\text{mv}]$$

For Si at $T = 300 \text{ k}$

$$\therefore r_{AC} \propto \frac{52}{I} \Omega \quad [\because \eta = 2]$$

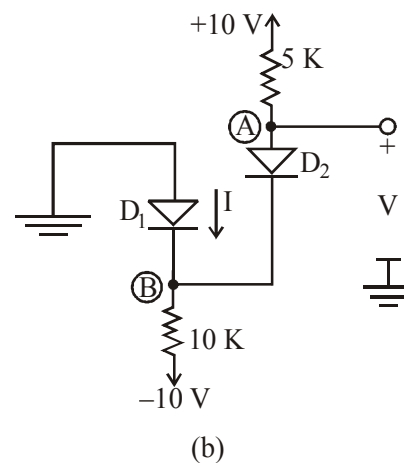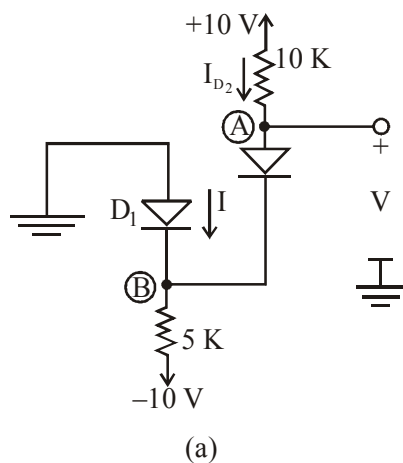Example 1 : Assume the Diode to be ideal, find the values of I and V in the circuit.



Note : In these circuits it might not be obvious at first sight whether none, one or both diode are conducting. In such cases we make a possible assumption, proceed with analysis, and then check whether we end up with consistent solution.

Solution : (a) Here we assume that both diodes are conducting. It follows that $V_B = 0$ and $V = 0$. The current through D_L can now be determined from

$$I_{D_2} = \frac{10 - 0}{10K} = 1 \text{ mA}$$

Writing a node equation at B,

$$I + 1 = \frac{0 - (-10)}{5}$$

results in $I = 1 \text{ mA}$.

Thus D_1 is conducting as originally assumed and final result is $I = 1 \text{ mA}$ and $V = 0 \text{ V}$.

(b) For this circuit, if we assume that both diodes are conducting, then $V_B = 0$ and $V = 0$. The current in D_2 is obtained from,

$$I_{D_2} = \frac{10 - 0}{5} = 2 \text{ mA}$$

node equation at B is,

$$I + 2 = \frac{0 - (-10)}{10}$$

$$I = -1 \text{ mA}$$

Which is not possible as this would mean that current in D_1 flows from n to p.

So, we start again, assuming that D_1 is OFF and D_2 is ON. The current I_{D_2} is given by,

$$I_{D_2} = \frac{10 - (-10)}{15} = 1.33 \text{ mA}$$


and voltage at node B is

$$V_B = -10 + 10 \times 1.33 = + 3.3 \text{ V}$$

Thus, D_1 is reverse biased and $I = 0$ and $V = 3.3 \text{ V}$.

Example 2 : Find I and V_0 , ideal diode is forward bias and short circuit.

Solution :

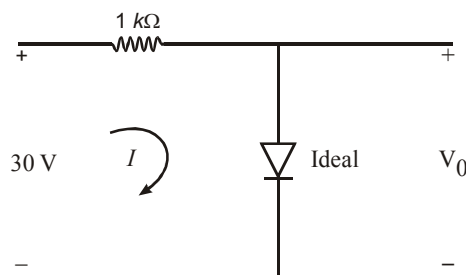


$$I = \frac{30}{1K} = 30 \text{ mA}$$

$$V_0 = 0 \text{ Volt}$$

Example 3 : Find I and V_o , ideal diode is forward bias and short circuit.

Solution :

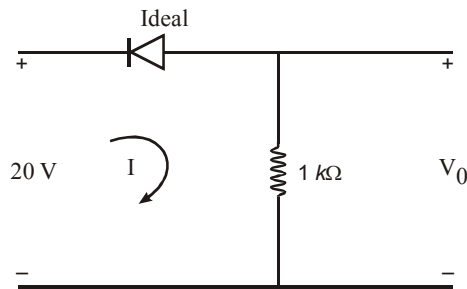


$$V_o = -20V$$

$$I = \frac{-20}{1K} = -20 \text{ mA}$$

Example 4 : Find V_o , I , I_D and I_R , Ideal diode is forward bias and short circuit.

Solution :

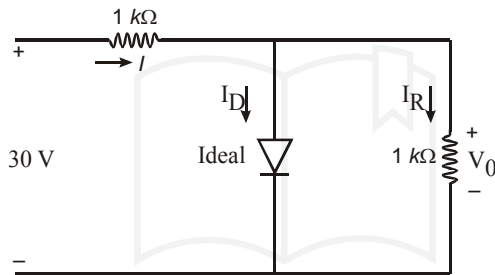

$$V_o = 0$$


$$I_R = 0$$

$$I_D = \frac{30V}{1K} = 30 \text{ mA}$$

$$I = I_D = 30 \text{ mA}$$

Example 5 : Find V_o , I , I_D and I_R , ideal diode is reverse bias and output current.

Solution :

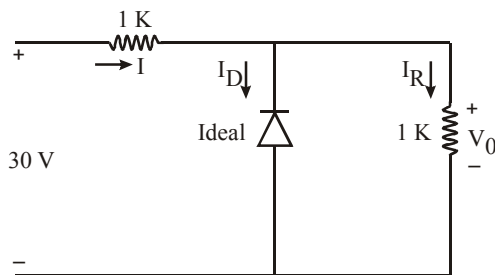


$$I_D = 0$$

$$I = I_R = \frac{30}{1K + 1K} = 15 \text{ mA}$$

$$V_o = 30 \times \frac{1}{1+1} = 15V$$

Example 6 : Find I and V_0 . Ideal diode forward bias and SC.

Solution :

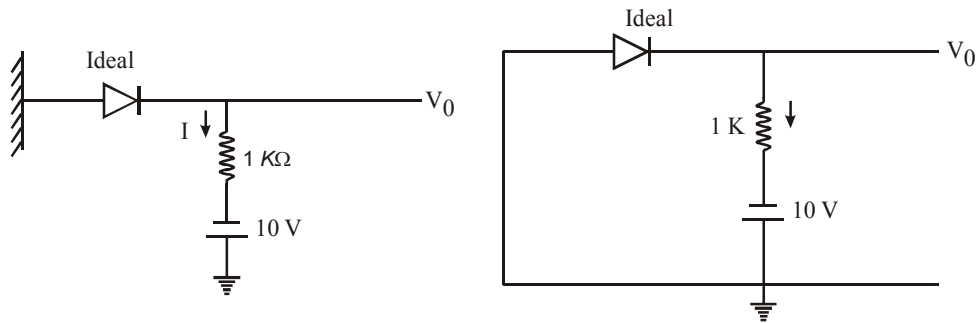


\therefore Ideal diode is forward bias and short circuit

$$\therefore V_0 = 0$$

$$\text{and } 0 - I \times 1K + 10V = 0$$

$$I = \frac{10}{1K} = 10\text{mA}$$

Example 7 : Find Z_{AB}

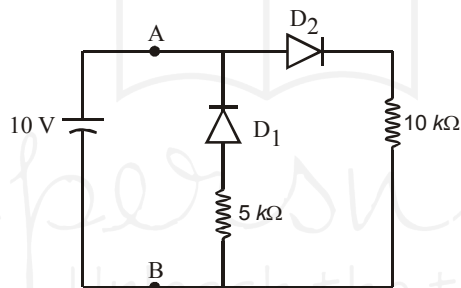


Solution : A is positive w.r.t. B.

D_1 is reverse bias and open circuit


D_2 is forward bias and short circuit.

$$Z_{AB} = 10k\Omega$$

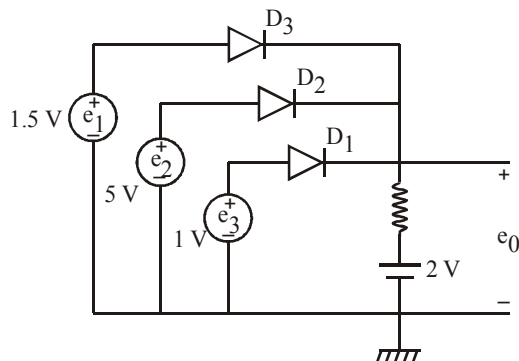Example 8 : Find which diode is conducting in the given circuit and also find e_0 .



Solution :

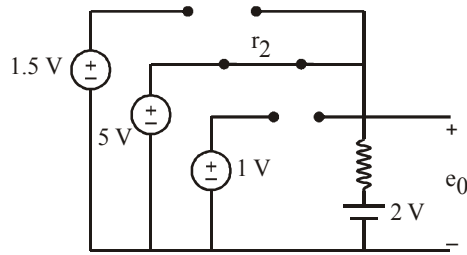


D_1 and D_3 are in reverse bias.

D_2 is forward bias and conducting.

$$e_0 = 5V$$

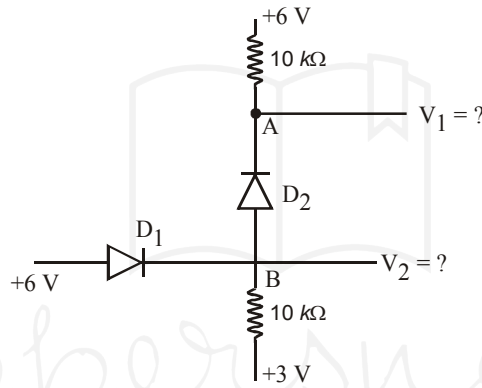
Example 9 : Find the voltage V_1 and V_2 of the arrangement given in the figure respectively :




Solution : At node A voltage is less than 6 volt due to drop in resistor $10\text{ k}\Omega$. So diode D_2 is forward bias and SC.

$$\therefore V_1 = V_2 = 6V$$

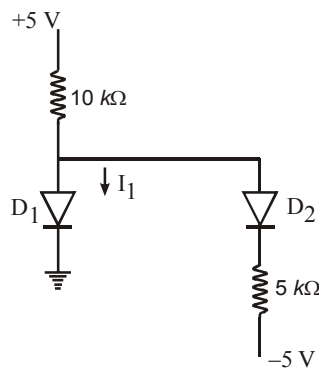Example 10 : If D_1 and D_2 are ideal diode find the current I_1 .




Solution :

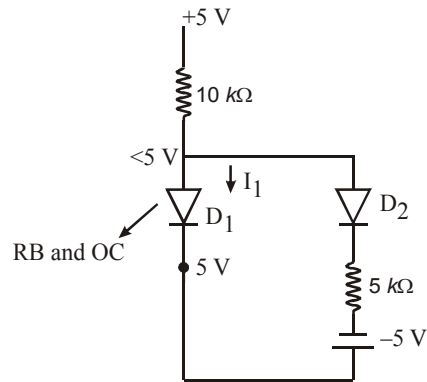

From the figure D_1 is reverse bias and open circuit.

$\therefore I_1 = 0$

Example 11 :

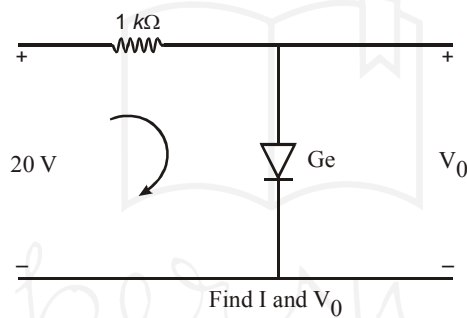


Find I and V_0 , Ge diode is forward bias.

Solution : $V_0 = V_{Ge} = 0.2V$

$$I = \frac{20 - V_{Ge}}{1K} = \frac{20 - 0.2}{1K} = 19.8 \text{ mA}$$


Example 12 : Find I and V_0 .

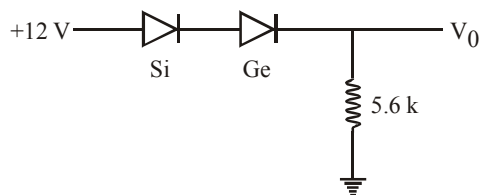


Solution :

$$I = \frac{12 - 0.7 - 0.2}{5.6K} = 1.982 \text{ mA}$$

$$V_0 = 12 - 0.7 - 0.2 = 11.1 \text{ Volt}$$

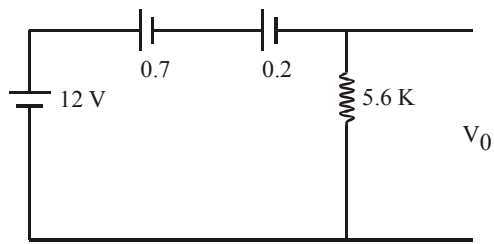


Example 13 : Find I and V_0 .

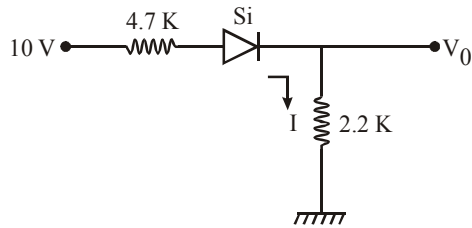


Solution :
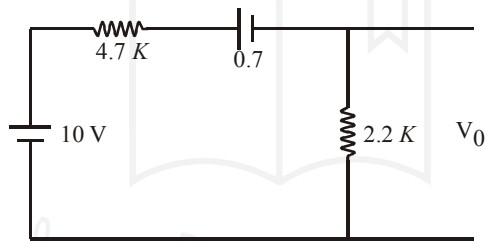
$$I = \frac{10 - V_r}{4.7\text{ K} + 2.2\text{ K}} = \frac{10 - 0.7}{4.7\text{ K} + 2.2\text{ K}} = 1.347\text{ mA}$$



$$V_0 = 1.347 \times 2.2 = 2.965\text{ V}$$


Example 14 : Find I and V_0 .

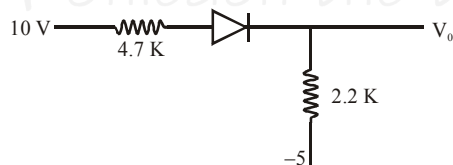


Solution :

$$I = \frac{10 - 0.7 + 5}{(4.7 + 2.2)\text{ K}} = 2.072\text{ mA}$$

$$V_0 = I \times (2.2\text{ K}) - 5 = 2.072\text{ mA} \times 2.2\text{ K} - 5 = -0.4416\text{ Volt}$$

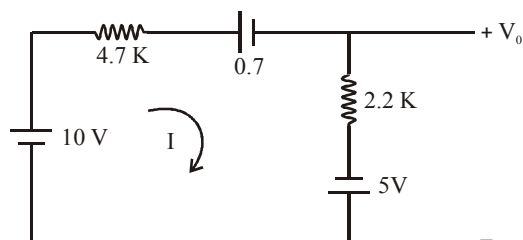


Example 15 : Find I

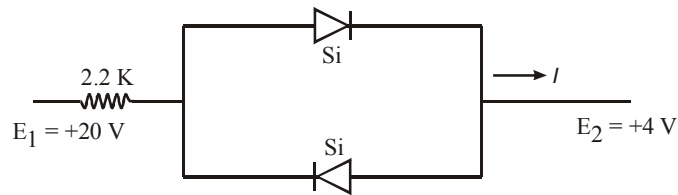


Solution : Since $E_1 > E_2$. Bottom diode is reverse bias and open circuit upper diode is forward bias and SC.


$$I = \frac{20 - 0.7 - 4}{2.2K} = 6.95 \text{ mA}$$

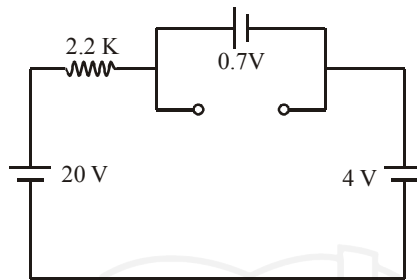

Example 16 : Find V_0 .

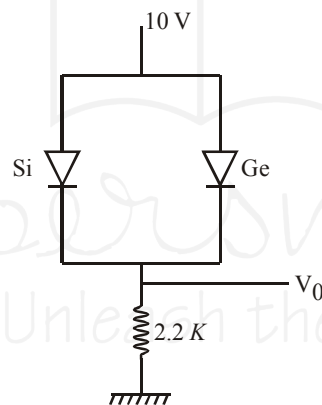

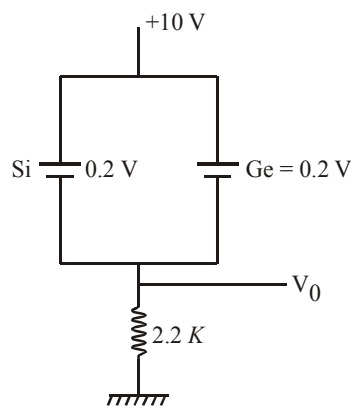
Solution : When 10 V is applied both Ge and Si diode both are forward bias and due to smaller cut in voltage Ge will enter into conduction.



$$V_0 = 10 - V_{Ge} = 10 - 0.2 = 9.8V$$

Si diode is forward bias but not conducting as the forward voltage is less than cut in voltage.

Example 17 : Find I_D .

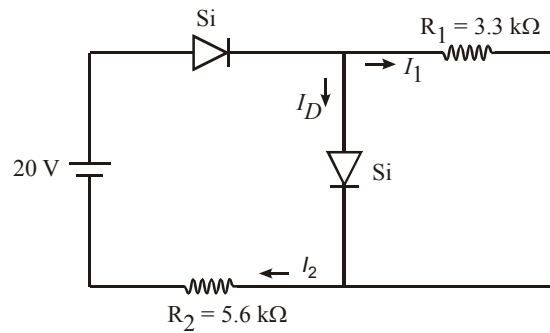


Solution :

$$V_{R_1} = V_{rSi} = 0.7V$$


$$I_1 = \frac{0.7}{3.3K} = 0.212 \text{ mA}$$
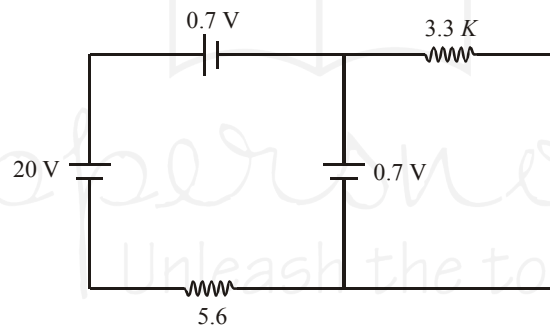
$$I_2 = \frac{20 - 0.7 - 0.7}{5.6} = 3.321 \text{ mA}$$



$$I_D = I_2 - I_1 = 3.321 - 0.212 = 3.109 \text{ mA}$$


Example 18 : Find V_{01} and V_{02} .

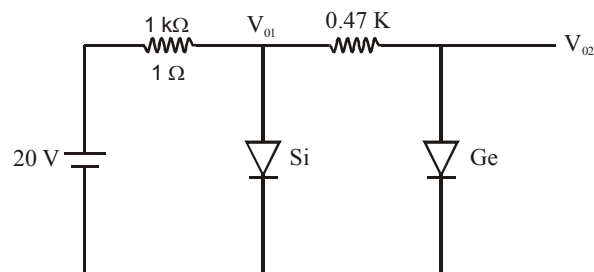


Solution :

$$V_{01} = 0.7V = V_{rSi}$$

$$V_{02} = 0.2V = V_{rGe}$$

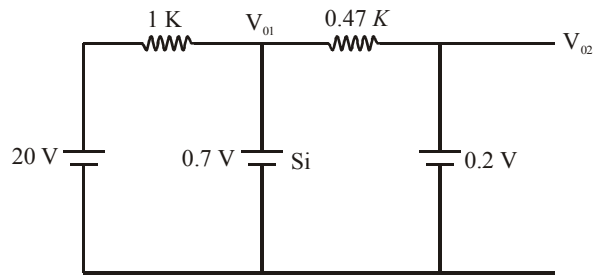


Example 19 : Find I_1 , I_2 and I_D .

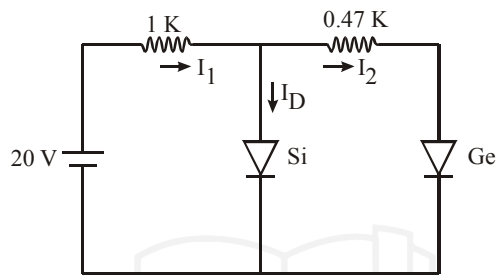

Solution :

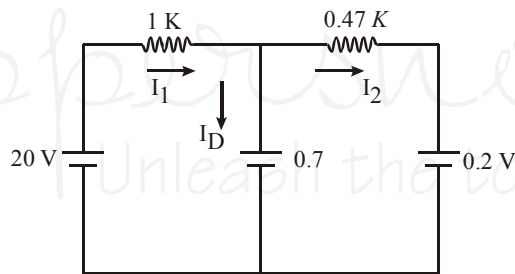
$$I_1 = \frac{20 - 0.7}{1K} = 19.3 \text{ mA}$$




$$I_2 = \frac{0.7 - 0.2}{0.47K} = 1.063 \text{ mA}$$

$$I_D = 19.3 \text{ mA} - 1.063 \text{ mA} = 18.237 \text{ mA}$$

Example 20 : Find I , V_1 and V_0 .

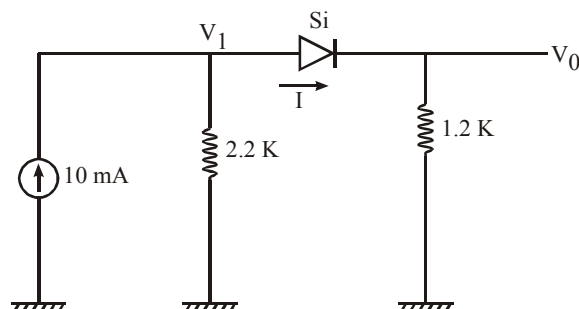

Solution :

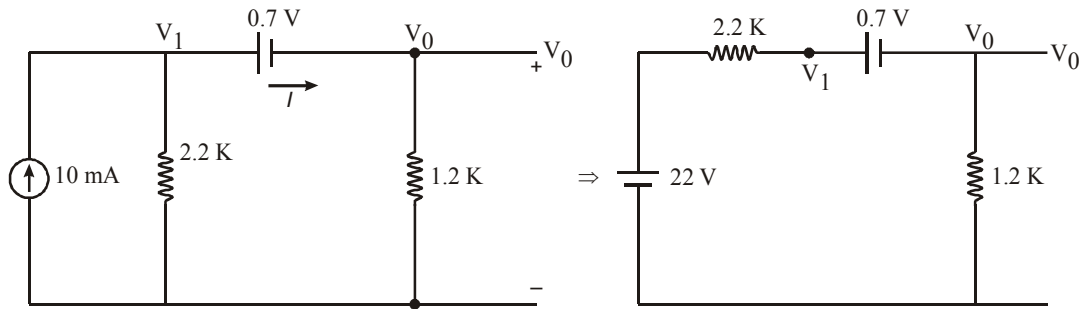

$$I = \frac{22 - 0.7}{2.2\text{K} + 1.2\text{K}} = 6.26 \text{ mA}$$


$$V_0 = I \times 1.2 \text{ K} = 6.26 \times 1.2 = 7.51 \text{ Volt}$$

$$V_1 = 22 - (2.2 \times 6.26) = 8.228 \text{ Volt}$$


or

$$V_0 = V_1 - V_{rSi} = 8.228 - 0.7 = 7.51 \text{ Volt}$$

Example 21 : Find V_0 and I_1 .

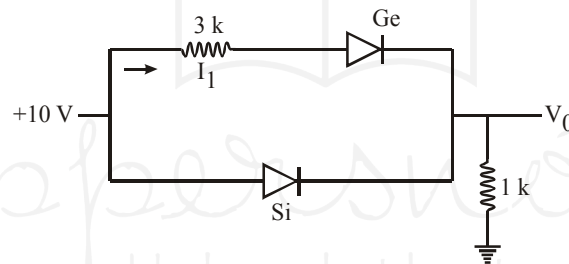

Solution :

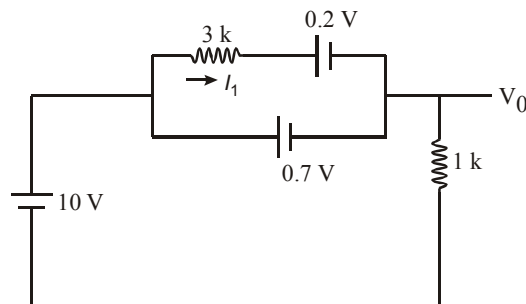


$$V_{rSi} = V_{rGe} + 3 \times I_1 \Rightarrow 0.7\text{V} = 0.2\text{V} + 3 \times I_1$$


$$I_1 = \frac{0.5}{3} = 0.166 \text{ mA}$$

$$V_0 = 10 - V_{rSi} = 10 - 0.7 = 9.3 \text{ Volt}$$

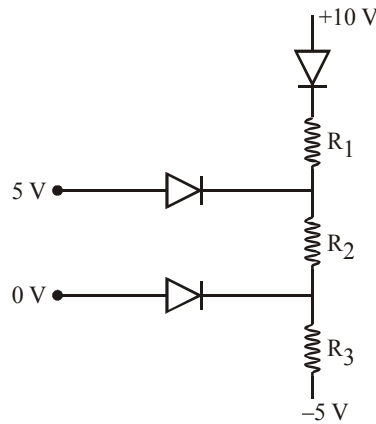Example 22 : The cut in voltage for each diode is 0.6 volt and each diode current is 0.5 mA. Find the values of R_1 , R_2 and R_3 .



Solution :

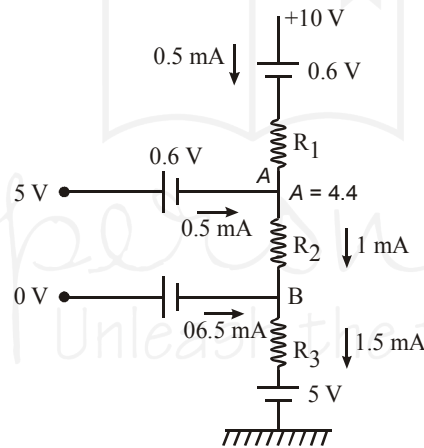

$$V_A = 5 - V_r = 5 - 0.6 = 4.4 \text{ Volt}$$

$$V_B = 0 - 0.6 = -0.6 \text{ Volt}$$

$$V_{AB} = V_A - V_B = 4.4 - (-0.6) = 5V$$

$$R_1 = \frac{10 - V_r - V_A}{0.5 \text{ mA}} = \frac{10 - 0.6 - 4.4}{0.5 \text{ mA}} = 10 \text{ k}\Omega$$

$$R_2 = \frac{V_A - V_B}{1 \text{ mA}} = \frac{5V}{1 \text{ mA}} = 5 \text{ k}\Omega$$


$$R_3 = \frac{V_B - (-5)}{1.5} = \frac{-0.6 + 5}{1.5} = 2.93 \text{ k}\Omega$$

1.3 CLIPPERS

Clippers are networks that employ diodes to “clip” away a portion of an input signal without distorting the remaining part of the applied waveform.


(i) Positive Clippers :

Circuit - 1 :

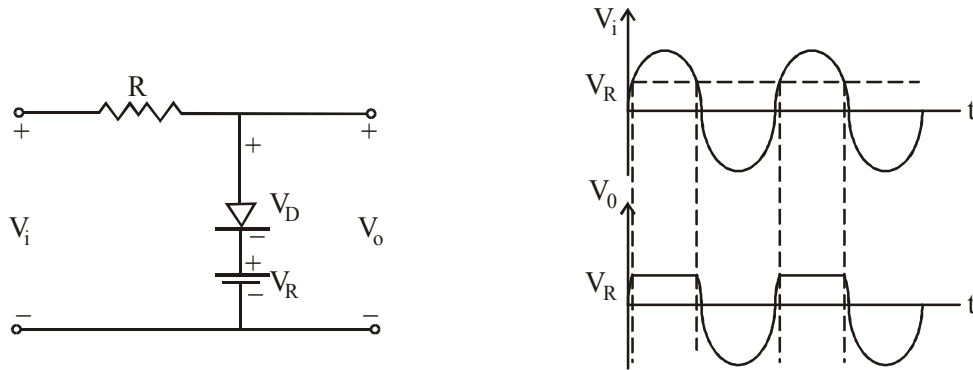

V_i	Diode	V_o
$V_i < V_R$	OFF	V_i
$V_i > V_R$	ON	V_R

Circuit - 2 :

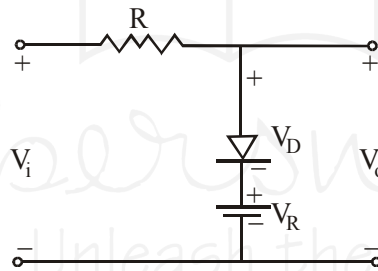


When $V_D > 0$ or $V_i < -V_R$, Diode \rightarrow OFF

$$V_o = V_i$$


When $V_D < 0$ or $V_i > -V_R$, Diode \rightarrow ON

$$V_o = -V_R$$

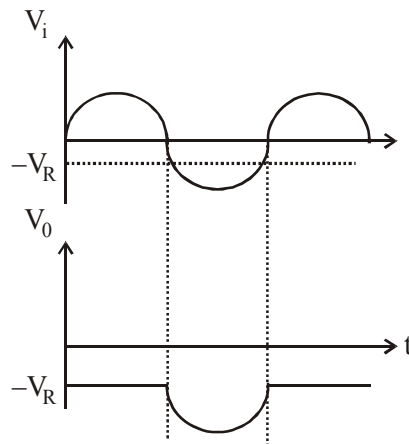

(ii) Negative Clippers :

Circuit - 1 :

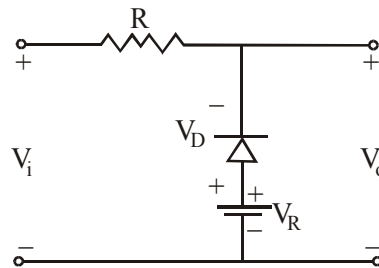


When $V_i > V_R$ Diode \rightarrow OFF


$$V_o = V_i$$

When $V_i < V_R$ Diode \rightarrow ON

$$V_o = V_R$$

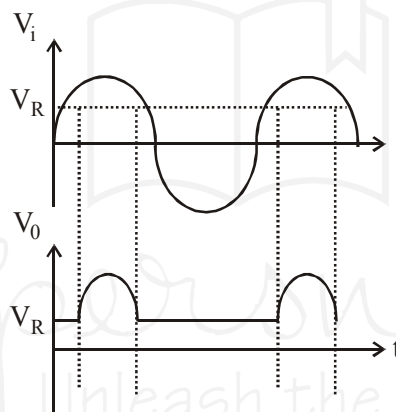

Circuit - 2 :

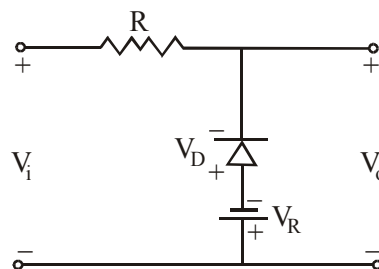


When $V_i < -V_R$, Diode \rightarrow ON

$$V_o = -V_R$$

When $V_i > -V_R$ Diode \rightarrow OFF

$$V_o = V_i$$

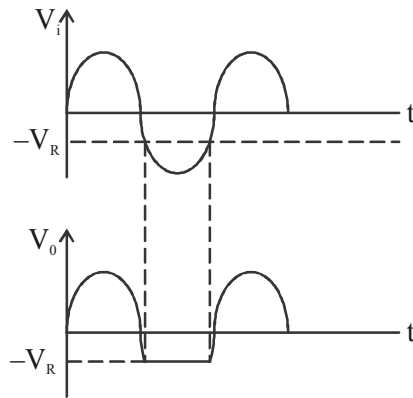


Some other types of Clipper Circuit :

Type - 1 :


When $V_i > V_R$ Diode \rightarrow ON $V_o = V_i$

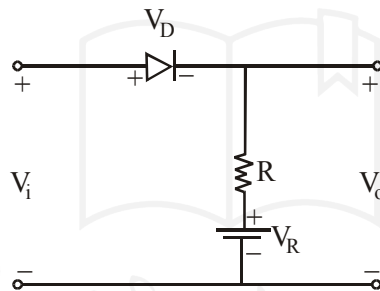When $V_i < V_R$ Diode \rightarrow OFF $V_o = V_R$



$$V_i = V_D + V_R$$

$$V_D = V_i - V_R$$

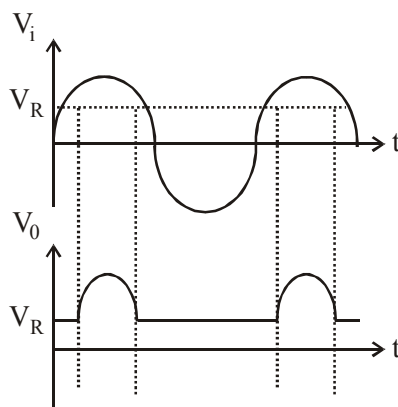

Type - 2 :

When $V_i > -V_R$, Diode \rightarrow ON $V_o \rightarrow V_i$

When $V_i < -V_R$, Diode \rightarrow OFF $V_o \rightarrow -V_R$